

2-2-E



Mahindra University Hyderabad
École Centrale School of Engineering
End-semester Examination

Program: B. Tech.

Branch: CM

Year: II

Semester: II

Subject: Computer Organization (MA2211)

Date: 03/06/2025

Start Time: 10:00 AM

Time Duration: 3 Hours

Max. Marks: 100

Instructions:

- 1) Answer all the questions.
- 2) All questions are self-explanatory; no clarification will be provided during the exam.

1. (20 points) Consider the following Boolean function:

$$F(A, B, C, D) = \sum(0, 2, 5, 7, 10, 13).$$

- (a) Express $F(A, B, C, D)$ in a truth table.
- (b) Find the complement $\overline{F}(A, B, C, D)$.
- (c) Show that $F + \overline{F} = 1$.
- (d) Express F and \overline{F} in Sum of Products (SOP) form.
- (e) Minimize F and \overline{F} using a Karnaugh Map (K-map).
- (f) Draw the logic circuit diagram for F and \overline{F} using basic gates (AND, OR, NOT).

2. (20 points) Consider the Boolean function of four variables, given by

$$F(A, B, C, D) = \sum(1, 4, 5, 7, 9, 12, 13).$$

Answer the following:

- (a) Implement the function F using a 4×1 multiplexer with A and B as the select lines and express the data inputs in terms of C and D .
 - (b) Implement the function F using a 4×1 multiplexer with C and D as the select lines and express the data inputs in terms of A and B .
 - (c) Implement the function F using an 8×1 multiplexer with A , B , and C as the select lines and express the data inputs in terms of D .
 - (d) Implement the function F using an 8×1 multiplexer with B , C , and D as the select lines and express the data inputs in terms of A .
3. (20 points) Design a combinational circuit that converts a 4-bit Binary Coded Decimal (BCD) input into a corresponding 7-segment display output. The circuit should take a 4-bit input A, B, C, D representing decimal digits 0 through 9. The output should control a 7-segment display using outputs a, b, c, d, e, f, g to correctly display the digit.
 - (a) Complete the truth table showing the relationship between the 4-bit BCD inputs and the corresponding 7-segment outputs for digits 0 through 9.
 - (b) For each output segment a, b, c, d, e, f, g , derive the Boolean expression using the truth table.
 - (c) Minimize the expression for a, b, c, d, e, f, g using a Karnaugh Map (K-map) and don't care conditions.
 - (d) Draw a logic diagram for the segments d, e, f using basic gates.

4. (20 points) Convert the following numbers from the given base to the other three bases listed in the table:

Decimal	Binary	Octal	Hexadecimal
154.625	—	—	—
—	1101011.011	—	—
—	—	475.4	—
—	—	—	2F9.B

Fill in the table by converting each number into the remaining three number systems and justify your answers.

5. (20 points) (a) Find the base r such that the following equation holds:

$$((24)_r + (13)_r) \times (11)_r = (561)_r$$

Interpret all numbers as base- r representations and perform the computations in decimal.

- (b) Represent the decimal numbers 794 and 735 in Binary Coded Decimal (BCD), and then find their sum.
- (c) Write the 4-bit Gray code representation for all decimal numbers from 0 to 15.
- (d) Let $A = 54$ and $B = 63$. Represent both numbers in 8-bit binary, then use 2's complement method to compute $A - B$ and $B - A$. Show all steps and express the final answer in decimal.
- (e) Perform the multiplication $(462)_8 \times (55)_8$.
- (f) Perform the addition $(5EF)_{16} + (EF6)_{16}$.