

**Mahindra University Hyderabad**  
**École Centrale School of Engineering**  
**End-semester Regular Examination**

**Program: B.Tech.    Branch: Computation & Mathematics    Year: Second    Semester: Second**  
**Subject: Computer Organization (MA 2211)**

**Date: 30/05/2024**  
**Time Duration: 03: 00 Hours**

**Start Time: 10: 00 PM**  
**Max. Marks: 100**

**Instructions:**

- 1) All questions are compulsory.
- 2) Start each answer on a new page and number your answers clearly. Answer all parts of the same question together and in sequence.
- 3) An explanation of every step is essential. Correct outcomes without description will not be evaluated.

**Q 01:** Select the correct choice for the following questions with a proper explanation.  
Correct choices without valid justification will not be considered. [02 × 15]


A) Complement of the expression  $A'B + CD'$  is \_\_\_\_\_.

- |                        |                        |                         |
|------------------------|------------------------|-------------------------|
| i) $(A' + B)(C' + D)$  | ii) $(A + B')(C' + D)$ | iii) $(A' + B)(C + D')$ |
| iv) $(A + B')(C + D')$ | v) None of these       |                         |

B) One of De Morgan's theorems states that  $(A + B)' = A' \cdot B'$ . Simply stated, this means that logically, there is no difference between:

- i) A NOR and an AND gate with inverted inputs
- ii) A NAND and an OR gate with inverted inputs
- iii) An AND and a NOR gate with inverted inputs
- iv) A NOR and a NAND gate with inverted inputs

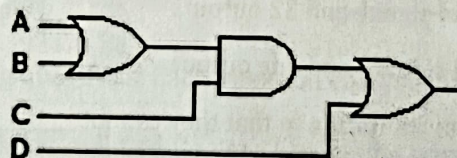C) The Boolean expression for the following logic circuit can be given as:



- |                   |                  |                     |
|-------------------|------------------|---------------------|
| i) $CA + CB + CD$ | ii) $CA + BD'$   | iii) $C(A + B) + D$ |
| iv) $CA + CB + D$ | v) None of these |                     |

D) The Boolean function  $AB + AC$  is equivalent to \_\_\_\_\_.

- |                         |                            |                          |
|-------------------------|----------------------------|--------------------------|
| i) $AB + AC + BC$       | ii) $A'B'C' + ABC' + A'BC$ | iii) $ABC + A'BC + B'C'$ |
| iv) $ABC + ABC' + AB'C$ | v) None of these           |                          |



E) The expression for Absorption law is given by \_\_\_\_\_.

i)  $A + AB = A$

ii)  $A + AB = B$

iii)  $AB + AA' = A$

iv)  $A + B = B + A$

v) None of these

F) Consider the Boolean function  $Y = (a + bc) \cdot (pq + r)$ . The complement of Y, i.e.,  $Y'$  is:

i)  $(a' + b'c') \cdot (p'q' + r')$

ii)  $a'(b' + c') + (p' + q')r'$

iii)  $(a' + b'c') + (p'q' + r')$

iv)  $(a'b'c') + (p'q'r')$

G) There are \_\_\_\_\_ minterms for four variables (a, b, c, d).

i) 0

ii) 2

iii) 4

iv) 8

v) None of these

H) The expression  $Y = AB + BC + AC$  shows the \_\_\_\_\_ operation.

i) EX-OR

ii) SOP

iii) POS

iv) NOR

v) None of these

I) Determine the values of A, B, C, and D that make the sum term  $A' + B + C' + D$  equal to zero.

i)  $A = 1, B = 0, C = 0, D = 0$

ii)  $A = 1, B = 0, C = 1, D = 0$

iii)  $A = 0, B = 1, C = 0, D = 0$

iv)  $A = 1, B = 0, C = 1, D = 1$

J) Total number of inputs in a half adder is \_\_\_\_\_

i) 2

ii) 3

iii) 4

iv) 1

v) None of these

K) A 32 to 1 multiplexer has the following terminals:

i) 32 outputs, one input, and 5 control signals

ii) 32 inputs, one output, and 5 control signals

iii) 5 inputs, one control signal, and 32 outputs

iv) 5 inputs, 32 control signals, and one output

L) Half-adders have a major limitation in that they cannot \_\_\_\_\_

i) Accept a carry bit from a present stage

ii) Accept a carry bit from the next stage

iii) Accept a carry bit from a previous stage

iv) Accept a carry bit from the following stages

M) Both OR and AND gates can have only two inputs.

i) True

ii) False



N) How many input lines are in a 'Full Adder'?

i) 2

ii) 4

iii) 1

iv) 3

v) None of these

O) What is a multiplexer?

i) It is a type of decoder which decodes several inputs and gives one output

ii) A multiplexer is a device which converts many signals into one

iii) It takes one input and results into many output

iv) It is a type of encoder which decodes several inputs and gives one output

Q 02: Answer the following questions. Each question consists of six marks. [06 × 05]



A) Design a combinatorial circuit with two inputs, which produce output as logic 0 when any one input is 1.

B) Create a circuit that needs to be built that produces an output of 1 if the decimal digit is 5 or greater, i.e.,  $\geq 5$ , and an output of 0 if the decimal digit is less than 5. How can this circuit be built using OR, AND, and inverters?

C) Multiply  $(11010.1110)_2$  by  $(1011.1101)_2$ . Also, divide the octal number  $(2276)_8$  by  $(102)_8$ . Show the calculation part.

D) Explain Binary Coded Decimal (BCD). Convert  $(237574)_8$  into BCD code. What are six illegal combinations in the BCD code? Explain why they are illegal.

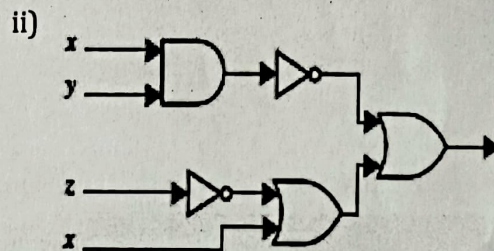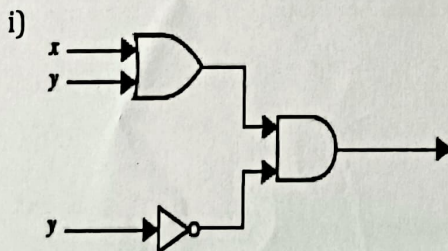E) Find the output of the given circuits.



Q 03: Answer the following questions. Each question consists of ten marks. [10 × 04]

A) Write the truth table and simplified Boolean expression with four inputs and one output for the following instances. Finally, design the combinational circuit for them.

i) The output is 1 when the binary value of the inputs is less than or equal to five.

ii) The output is 1 when the binary value of the inputs is greater than or equal to ten.

B) What is K-map? Demonstrate the K-map used for three variables, x, y, z, and for four variables, w, x, y, z. Finally, use K-maps to minimize the following Sum of Product expansions.



i)  $F_1 = xy\bar{z} + x\bar{y}\bar{z} + \bar{x}yz + \bar{x}\bar{y}\bar{z}$

ii)  $F_2 = xy\bar{z} + x\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z}$

C) Explain the following by taking a suitable example. Also, give figures where it seems necessary.

i) Half Adder with designing and logic diagram.

ii) 3 to 8 Decoder with truth table and logic diagram.

D) Implement a converter, which converts a 4 – bit binary code WXYZ into its equivalent Gray code ABCD.