

**Mahindra University École Centrale School of Engineering  
Hyderabad**

Program: B.Tech.    Branch: AI/CSE/CM/CE/ME/MT/NT/CB/BT    Year: I    Semester: I  
End term Examination (Fractal)

Subject: EE1103 Introduction to Electrical Engineering

Date: 10.11.2022


Time: 02.00 PM to 04.00 PM

Time Duration: 2:00 Hours


Max. Marks: 100

Note: There are 5 questions, all of which are compulsory.

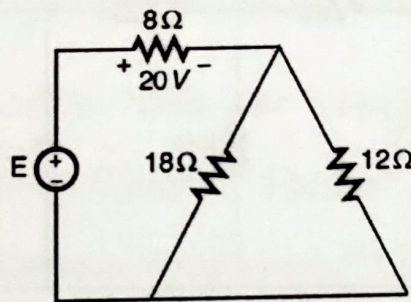
- Q 1/ (a) In the circuit below, determine the current *through the 12Ω resistor*. Also, calculate the supply voltage, *E*. (10 marks)



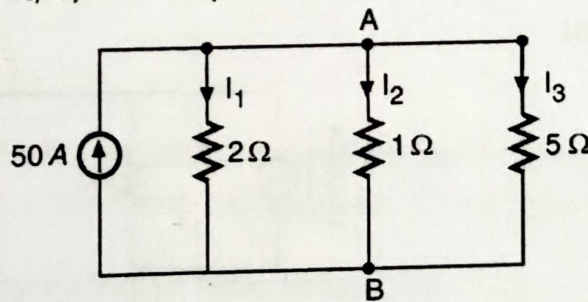- (b) In the circuit below, find  $I_1$ ,  $I_2$ , and  $I_3$ . (10 marks)




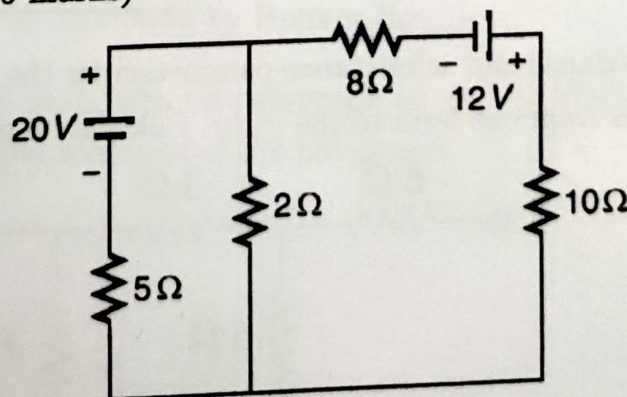- Q 2 Find the current flowing through the 10Ω resistor by first finding the *Thevenin equivalent circuit*. (20 marks)






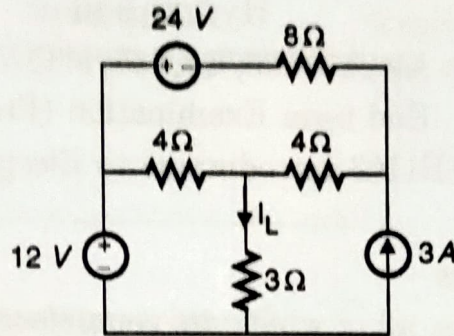
- Q 3 Use **superposition** to find the current through the  $3\Omega$  resistor. (You must use the principle of superposition only to solve this problem.) (20 marks)



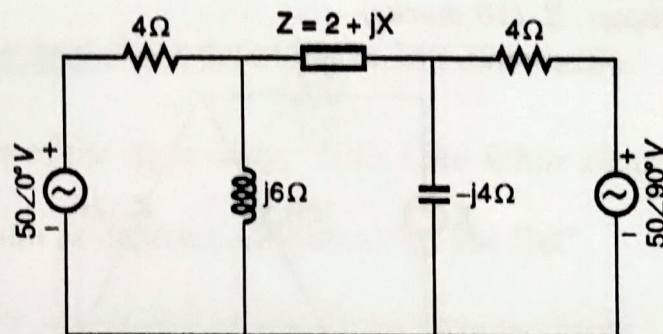- Q 4 (a)  $Z$  is the load and has a fixed resistance of  $2\Omega$  and a variable reactance  $jX$ . Determine the value of  $X$  for maximum power transfer to load. (10 marks)



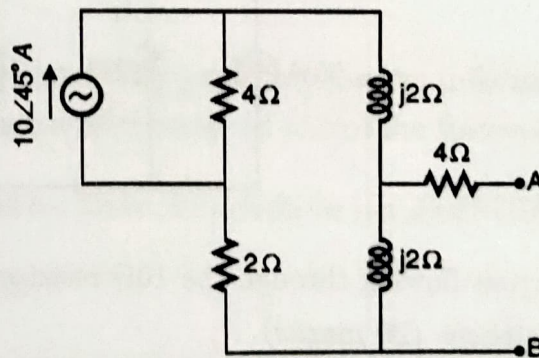- (b) Determine the **impedance** to be connected between A-B for maximum power transfer. (10 marks)



- Q 5 Find the **impedance** and **admittance** parameters for the given network. (Do not convert the parameters from one form to the other. Calculate both individually) (20 marks)

