



Mahindra University École Centrale School of Engineering
Hyderabad

Program: B.Tech.

Branch: Mechatronics

Year: II

Semester: II

Minor I Examination

Subject: EE2201 Digital Electronics


Date: 06.03.2023

Time Duration: 1:30 Hours

Time: 10.00 AM to 11.30 AM

Max. Marks: 60

Note: Use of calculator is not allowed.

Q 1	Use a Karnaugh map to reduce each expression to a minimum SOP form a. $A'B'C'D' + AC'D' + B'CD' + A'BCD + BC'D$ b. $x'z + w'xy' + w(x'y + xy')$ c. $A'B'C'D' + A'CD' + AB'D' + AFCD + A'BD$	(12)
Q 2	Use Quine McCluskey method to minimize $S = \sum (0, 1, 2, 4, 6, 8, 9, 11, 13, 15)$	(12)
Q 3	Design a combinational circuit with 4 inputs w, x, y, and z, and one output, f. The output "f" is one of the segments in the seven-segment display. w, x, y and z are BCD inputs. 	(12)
Q 4	For the Boolean function given by, $F = xy'z + x'y'z + w'xy + wx'y + wxy$ a. Obtain the truth table b. Use any technique to simplify the function to a minimum number of literals c. Obtain the truth table for the simplified function and compare to part(a) d. Draw the logic diagram of the simplified expression.	(12)
Q 5	Obtain both 1's and 2's complements of the following binary numbers i. 00010000 iii. 00000000 ii. 11011010 iv. 10101010	(12)

00100101

+1

110

01010101

+1

110110

11101111

+1

11110000

$A'BD + ABC' + B'D'$

11111111

+1

10000000