

**Mahindra University École Centrale School of Engineering  
Hyderabad**

Program: B.Tech. Branch: AI/CSE/CM/CE/ME/MT/NT/CB/BT  
End term Examination (Fractal)  
Subject: EE1105 (Electronics)

Year: I Semester: I

Date: **28.12.2022**

Time Duration: **2:00 Hours**


Time: **09.00 AM to 11.00 AM**

Max. Marks: **60**

Note: There are 5 questions, all of which are compulsory.


**Q1** In the circuit below, find  $V_R$ ,  $I_D$ . Given,  $V_D = 0.7V$ .

10

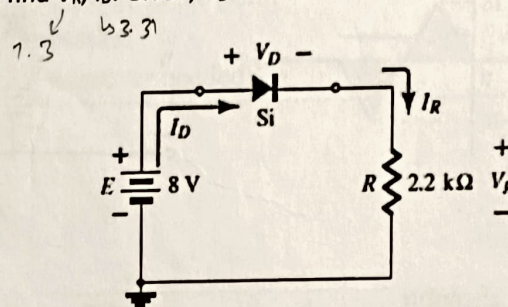


**Q2** Calculate the output voltage for the circuits below.

(a)

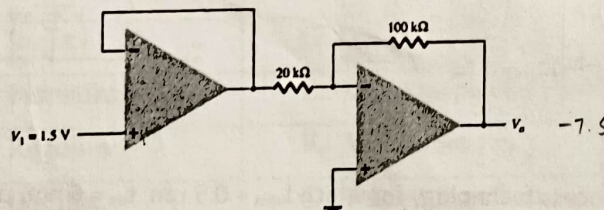

5

(b)

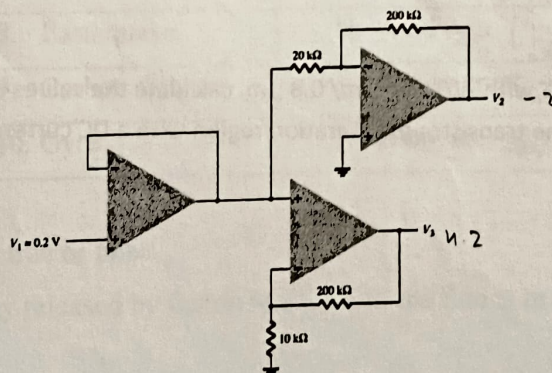

5

**Q3** Express the following numbers in decimal:

(a)  $(10110.0101)_2$  22.3125

(b)  $(16.5)_{16}$

(c)  $(26.24)_8$

10  
(2 x 5)



(d)  $(DADA.B)_{16} = 5602.6675$

(e)  $(1010.1101)_2 = 10.6125$



Q4 Simplify the Boolean expression using a 4-variable k-map.

10

$$F(A, B, C, D) = \sum (0, 1, 2, 5, 8, 9, 10) \quad \bar{B}\bar{C} + \bar{B}\bar{D} + \bar{A}\bar{C}\bar{D}$$



Q5 Draw the output waveform for the following diode circuits (Si diodes with  $V_k = 0.7V$ )

(a)

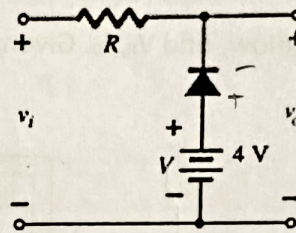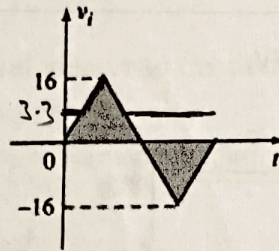

5

(b)

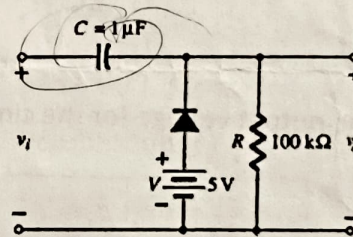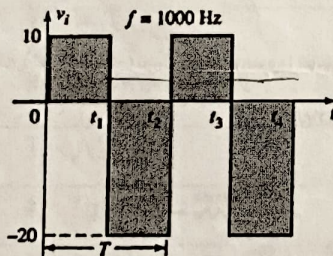

5

Q6 Consider a process technology for which  $L_{min} = 0.5 \mu m$ ,  $t_{ox} = 6 nm$ ,  $\mu_n = 350 cm^2/V \cdot s$ , and  $V_t = 0.7 V$ .

10

(3+7)

(a) Find  $C_{ox}$  and  $k_n \rightarrow 5.75 \times 10^{-3}$

(b) For a MOSFET with  $W/L = 8 \mu m / 0.8 \mu m$ , calculate the values of  $V_{ov}$ ,  $V_{GS}$ ,  $V_{DSmin}$  needed to operate the transistor in saturation region with a DC current -  $I_D = 100 \mu A$ .